

University of Moratuwa

Department of Electronic and Telecommunication
Engineering

EN3023 - Electronic Design Realization



Project report- Imposters

Name	Index Number
C.N. Abeywansa	190005E
W.A.D.K. De Silva	190128H
M.S.K. Gunasekara	190202F
G. I. Hewasura	190234E

February 13, 2023

Contents

Instruction Set Architecture	
Main controller	4
Instruction passer	6
ALU controller	6
Arithmetic and Logic Unit (ALU)	7
MUXs	9
Register File	11
Instruction Memory	11
Test bench	14
Appendix	17

Instruction Set Architecture

The ISA is a RISC-V architecture. 38 basic instructions are implemented including the U type and the J type. All instructions are 32 bit fixed length.

Instruction set

31	27	26	25	24	20	19	15	14	12	11	7	6	0	
funct7				rs2		rs1		funct3		rd		opcode		R-type
imm[11:0]						rs1		funct3		rd		opcode		I-type
imm[11:5]				rs2		rs1		funct3		imm[4:0]		opcode		S-type
imm[12 10:5]				rs2		rs1		funct3		imm[4:1 11]		opcode		B-type
imm[31:12]										rd		opcode		U-type
imm[20 10:1 11 19:12]										rd		opcode		J-type

R – type

R-type instructions are for register-register operations. R-type instructions specify two source registers (rs1 and rs2) and a destination register (rd). The funct10 field is an additional opcode field.

I – type

I- type instructions are for immediate and load operations. I-type instructions specify one source register (rs1) and a destination register (rd). The second source operand is a sign-extended 12-bit immediate, encoded contiguously in bits 21–10. The funct3 field is a second opcode field.

S-type

S-type instructions are for store operations.

B-type

B-type instructions are for conditional branch operations. The 12-bit immediate is sign-extended, shifted left one bit, then added to the current pc to give the target address.

U-type

U-type instructions are for incrementing the PC register by an immediate value specified by the instruction. A 20'b0 is added concatenated to the end of the immediate and added to the current PC value.


J-types.

Absolute jumps (J) and jump and link (JAL) instructions use the J-type format. The 25-bit jump target offset is sign-extended and shifted left one bit to form a byte offset, then added to the pc to form the jump target address. Jumps can therefore target a ± 32 MB range. JAL stores the address of the instruction following the jump (pc+4) into register x1

Instruction	Description
ADD	$rd = rs1 + rs2$
SUB	$rd = rs1 - rs2$
XOR	$rd = rs1 \wedge rs2$
OR	$rd = rs1 \vee rs2$
AND	$rd = rs1 \& rs2$
SLL	$rd = rs1 \ll rs2$
SRL	$rd = rs1 \gg rs2$
SRA	$rd = rs1 \gg rs2$
SLT	$rd = (rs1 < rs2)?1:0$
SLTU	$rd = (rs1 < rs2)?1:0$
ADDI	$rd = rs1 + imm$
XORI	$rd = rs1 \wedge imm$
ORI	$rd = rs1 \vee imm$
ANDI	$rd = rs1 \& imm$
SLLI	$rd = rs1 \ll imm[0:4]$
SRLI	$rd = rs1 \gg imm[0:4]$
SRAI	$rd = rs1 \gg imm[0:4]$
STLI	$rd = (rs1 < imm)?1:0$
SLTIU	$rd = (rs1 < imm)?1:0$
LB	$rd = M[rs1+imm][0:7]$
LH	$rd = M[rs1+imm][0:15]$
LW	$rd = M[rs1+imm][0:31]$
LBU	$rd = M[rs1+imm][0:7]$
LHU	$rd = M[rs1+imm][0:15]$
SB	$M[rs1+imm][0:7] = rs2[0:7]$

SH	$M[rs1+imm][0:15] = rs2[0:15]$
SW	$M[rs1+imm][0:31] = rs2[0:31]$
BEQ	if($rs1 == rs2$) PC += imm
BNE	if($rs1 != rs2$) PC += imm
BLT	if($rs1 < rs2$) PC += imm
BGE	if($rs1 >= rs2$) PC += imm
BLTU	if($rs1 < rs2$) PC += imm
BGEU	if($rs1 >= rs2$) PC += imm
JAL	rd = PC+4; PC += imm
LUI	rd = imm << 12
AUIPC	rd = PC + (imm << 12)

Main controller

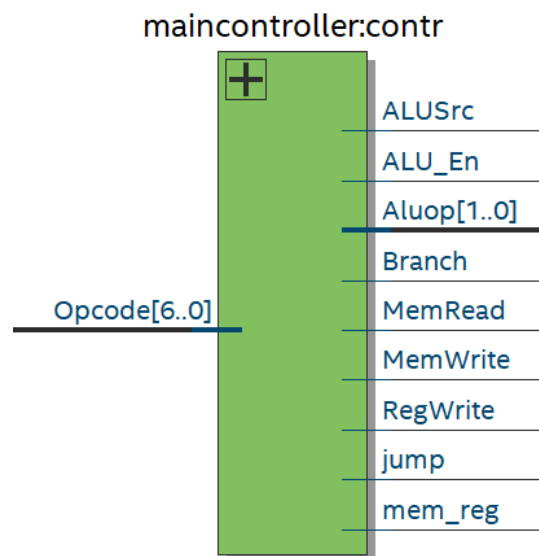


Main controller gets the opcode of the 32 bit instruction as the input from the Instruction passer and depending on the opcode the controller decides on 10 control signals and provides them to the specified modules through the data path. The 10 control signals are;

1. Register write
2. Mem- write

3. Mem- read
4. Branch
5. ALU Src
6. ALU op (2 bits)
7. J-type
8. ALU enable
9. Mem-to-Register


Instruction Type	Control signal
R- type	1000000000
I-type load	1010110000
I-type imm	1000101000
s-type	0100110001
sb-type	0001011000
jal-type	10001xx110
lui-type	10001xx010
auipc-type	00000xx010

Instruction passer

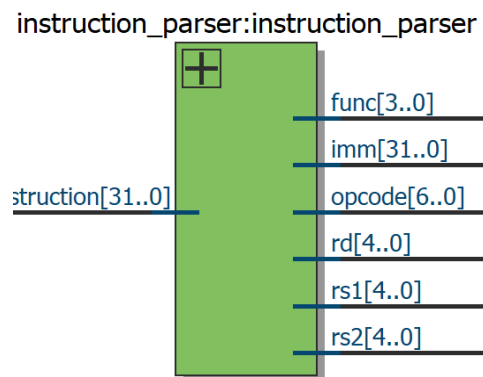


The input to the instruction passer is the 32 bit instruction straight from the instruction memory. Depending on the 7 bit Opcode of the instruction the instruction passer decides on the instruction type and outputs the values of the 5 bit read address 1, 5 bit read address 2, 5 bit write address to the register file and a 32 bit immediate value.

ALU controller

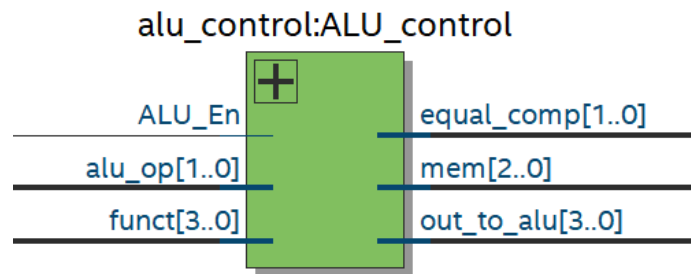

The ALU controller gets the 4 bit instruction[14:12,30] as an input from the instruction passer, and two control signals 1 bit ALUEn and 2 bit ALUOp from the maincontroller. Depending on the input bits the controller determines which operation should be performed by the ALU and pass it over to the ALU as the 4 bit ALU control signal 2 bit equal_comp bit. Another three bit control signal is passed over to the data memory which will decide whether to signed or unsigned versions of read word, half word or byte.

Arithmetic and Logic Unit (ALU)

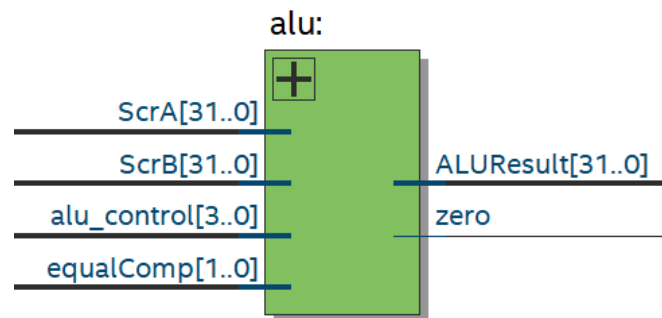

ALU is designed to perform operations between two 32 bit operands and produce 32 bit outputs. The control signals given as outputs from the ALU controller (4 bits) determines which operation will be performed on the operands. The 2 bit equal_comp input signal from the ALU controller determines which operation should be performed by the comparator part of the ALU. The table below contains the list of operations.

Operation	Control signal	Description
ADD	0010	Add the two operands
SUB	0110	Subtract the two operands

OR	0011	Perform OR operation between the two operands
AND	0000	Perform AND operation between the two operands
SLL	0100	Perform logical left shift on the operand ($op1 \ll op2$)
SRL	1000	Perform logical right shift on the operand ($op1 \gg op2$)
SLT	0101	Compare the two operands and write 1 to destination register if $op1 < op2$
SLTU	0111	Compare the unsigned versions of the two operands and write 1 to destination register if $op1 < op2$


Operation	Control signal (equal_comp)	Description
BEQ	11	Compares the two operands (perform XOR operation) and raise zero flag if the ALU result is 32'b0
BNE	01	Compares the two operands (perform XOR operation) and raise zero flag if the ALU result is not 32'b0
BLT	00	Perform subtraction and raise zero flag if the sign of ALU result is 1

BGE	10	Perform subtraction and raise zero flag if the sign of ALU result is
-----	----	--

Aside from the ALU result the ALU maintains a zero flag which will be used for branching instructions. The zero flag is set to one when the resultant from the ALU is 32'b0.


The ALU has two inputs to receive the two operands. One input is directly from the register file and the other input is connected to a MUX that allows to give the immediate from the instruction or the read value from the register depending on the control signal (ALUSrc) given to the MUX as the selection input.

AND Gate

 

The two inputs to the AND gate are zero flag from the ALU and the branching control signal from the main controller. Depending on the inputs the AND gate decides on whether to branch or not and pass a one bit input to the branching mux.

MUXs

 

J-Type selection MUX

The MUX gets two 32 bit inputs and a one bit control signal from the main controller as the control signal and outputs a 32 bit output to the write data input to the register file. The control signal choose either the PC-value+4 or the data memory output depending on the instruction type.

Control signal	MUX out
1	PC_value+4
0	Data memory output

ALU input selection MUX

The MUX gets two inputs, one from the Instruction passer (32 bit immediate value) and another 32 bit input from the register file. Depending on the control signal ALUSrc provided from the maincontroller the MUX chooses either of the inputs and pass it on to the ALU as the second operand.

Control signal	MUX out
1	Immediate value
0	Register file data

Branching MUX

The branching MUX gets the 32 bit current PC + 32 bit immediate value passed from the add only ALU and PC+4 value as the two inputs and choose either of them depending on the branching control signal provided as the output from the AND gate.


Control signal	MUX out
1	Immediate value + Current PC value
0	PC value + 4

Data memory MUX

The control signal memory to register given from the controller chooses the ALU result or the data read from the data memory and pass it on to the J-Type selection MUX.


Control signal	MUX out
1	Data memory output
0	ALU result

Register File

 


The register file was created with the ability to read two registers and write to one register in one clock cycle. Each register has a width of 32 bits. The register file contains 32 registers (x0 to x31), where x0 is a special read-only register called the Zero register, which always holds the value 0x00000000. Other 31 registers can be written and read as normal. The reg_write is used as a write enable switch to write the data in the write_data bus to the register specified by the address in the write_addr bus. read_data_1 and read_data_2 always output the data in the registers specified by read_addr_1 and read_addr_2, respectively. The reset pin sets all the registers to 0x00000000.

Instruction Memory

 

All the prefetched instructions are stored inside the instruction memory and the relevant address to be fetched will be provided by the program counter output. When the output of the program counter (pc_out) reaches the instruction memory and gets triggered by the positive edge of the clock the instruction in the relevant address will be sent out from the instruction memory to the instruction passer where all the decoding happens. In the instruction memory we designed we can hold a set of 32 instructions at a time. Since our instruction memory was word addressable, we had to shift the address always by two bits to cancel out the effect of incrementing the pc count by 4.


Data Memory

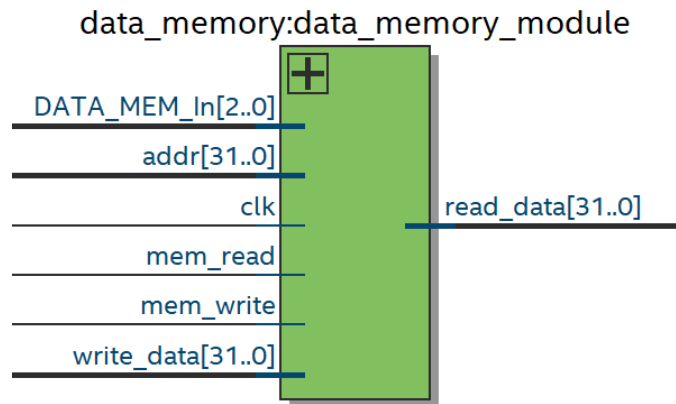


Data memory is the place where all the program executable operands are stored. In the data memory we designed we have 64 locations to store the data that comes to the data memory. There are 2 control signals which come to the data memory as mem_write and mem_read. And a three-bit signal is coming from the ALU (Arithmetic Logic Unit) control which is named as DATA_MEM_IN. The three bits in DATA_MEM_IN contains the signed unsigned identifying bit and two bits to distinguish whether the load or store data to be a byte, half word, or a word. If the mem_read signal is enabled the data will be sent from the data memory as preferred by the DATA_MEM_IN signal. If mem_write is enabled the data comes to the data memory from the register files will get stored in the relevant address (which is calculated by the ALU) by checking whether a byte, half word or a word needs to be stored.

Operation	Control Signal (DATA_MEM_IN)
Load Byte	001
Load Halfword	010
Load word	011
Load Byte Unsigned	101
Load Halfword Unsigned	110
Store Byte	001
Store Halfword	010
Store Word	011

Data path

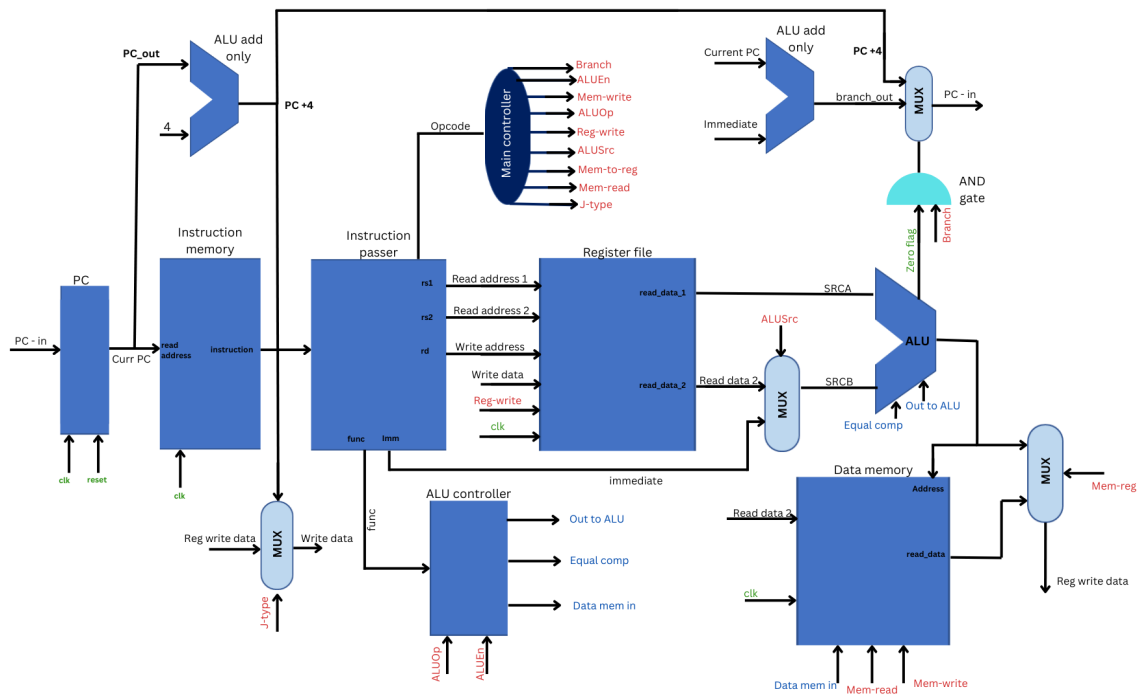

Test bench

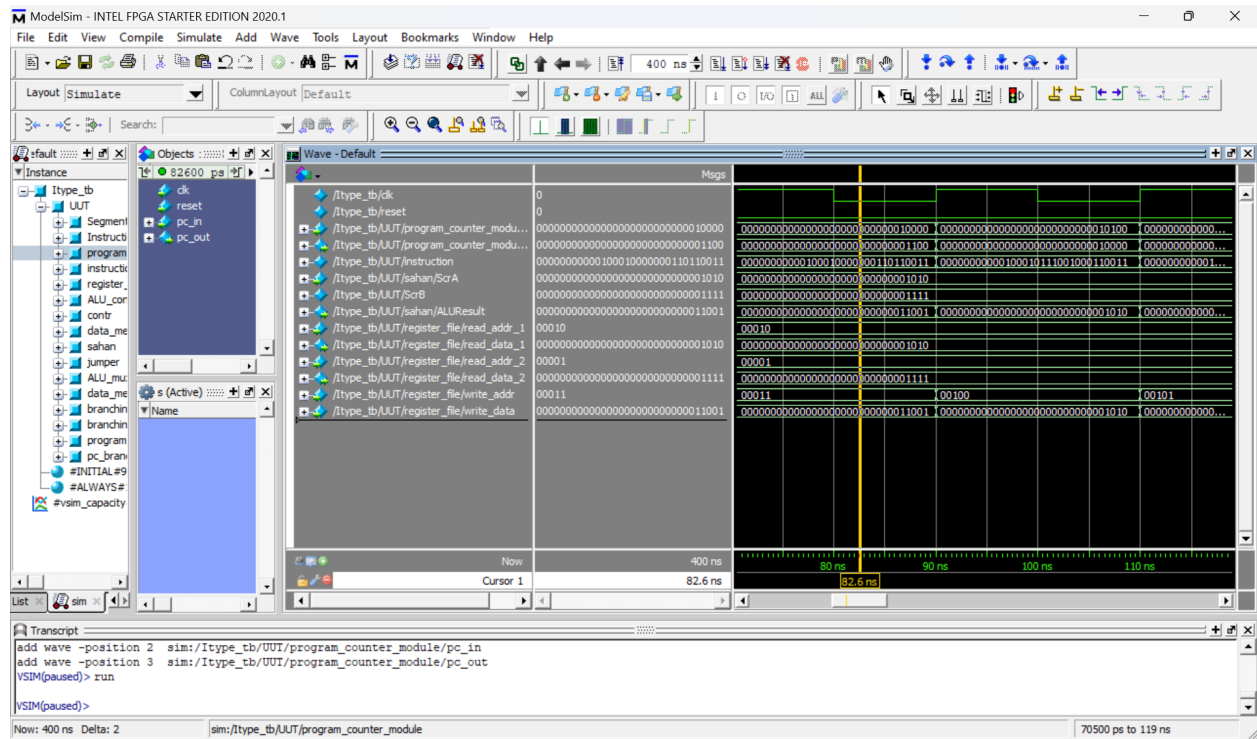

The test bench was coded with a time scale of 1 ns/ 100 ps. Initially, it resets the clock, and set the reset wire high for 15 ns. This allows to initialize the Program counter to run the first instruction. Then, it uses a timed loop to run the clock at 50 MHz. The following is the code used for the test bench.

```
`timescale 1ns/100ps

module main_tb;

reg clk,reset;

main UUT (clk, reset, ALU_result);

initial
begin
    clk = 0;
    reset = 1;
    #15;reset = 0;
    #400
    $stop;
    //$finish;
end
always begin #10 clk=~clk; end
endmodule
```


Appendix

```
// -----MAIN_CODE-----

`timescale 1ns/100ps

module Itype(input clk, input reset, output [6:0]HEX0,output [6:0]HEX1,output [6:0]HEX2,output
[6:0]HEX3,output [6:0]HEX4,output [6:0]HEX5,output [6:0]HEX6,output [6:0]HEX7);

    //PC pc (.clk(clk), .reset(rst))

    wire [31:0] instruction,ScrB,register_write_data;
        wire [1:0] Alu_op;
        wire [3:0] out_to_alu;
    wire [1:0] equal_comp;
        wire [2:0] mem;
        wire RegWrite, MemWrite, MemRead, branch, ALUSrc,jump, ALU_En,
mem_reg,zero,branch_zero;

        wire [4:0] read_addr_1;
        wire [4:0] read_addr_2;
        wire [4:0] write_addr;
        wire [31:0] write_data;
        wire [31:0] read_data_1;
        wire [31:0] read_data_2;
        wire [6:0] Opcode;
        wire [31:0] immidiate;
        wire [3:0] funct;
        wire [31:0] read_data;
        wire [31:0] branch_out;
        wire [31:0] ALU_result;

    // pc
        wire [31:0] pc_in;
        wire [31:0] pc_out;
        wire [31:0] pc_plus4;
```

```

segment Segment7(
.clk(clk),
.ALU_result(ALU_result),
.HEX0(HEX0),
.HEX1(HEX1),
.HEX2(HEX2),
.HEX3(HEX3),
.HEX4(HEX4),
.HEX5(HEX5),
.HEX6(HEX6),
.HEX7(HEX7)
);

    //wire reg_w;
instruction_memory Instruction_memory (
    .read_addr(pc_out),
    .clk(clk),
    .instruction(instruction)
);
program_counter program_counter_module (
    .clk(clk),
    .reset(reset),
    .pc_in(pc_in),
    .pc_out(pc_out)
);

instruction_parser instruction_parser(
    .instruction(instruction),
    .rs1(read_addr_1),
    .rs2(read_addr_2),
    .rd(write_addr),
    .opcode(Opcode),
    .imm(immediate),
    .func(func)
);

    // for R type instruction

```

```

register_file register_file(
    .clk(clk),
    .read_addr_1(read_addr_1),
    .read_addr_2(read_addr_2),
    .write_addr(write_addr),
    .write_data(write_data),//.....
    .reg_write(RegW),
    .read_data_1(read_data_1),
    .read_data_2(read_data_2)
);

```

```

alu_control ALU_control (
    .funct(funct),
    .alu_op(Alu_op),
    .out_to_alu(out_to_alu),
    .ALU_En(ALU_En),
    .equal_comp(equal_comp),
    .mem(mem)

);

```

```

maincontroller contr(
    .Opcode(Opcode),
    .RegWrite(RegW),
    .MemWrite(MemW),
    .MemRead(MemR),
    .Branch(branch),
    .ALUSrc( ALUSrc),
    .Aluop(Alu_op),
    .jump(jump),
    .ALU_En(ALU_En),
    .mem_reg(mem_reg)
);

```

```

data_memory data_memory_module(
    .clk(clk),
    .mem_read(MemR),
    .mem_write(MemW),
    .DATA_MEM_In(mem),
    .read_data(read_data),
    .write_data(read_data_2),
    .addr(ALU_result)
    // Add other inputs and outputs here
);

```

```

alu ALU(
    .ScrA(read_data_1),
    .ScrB(ScrB),
    .alu_control(out_to_alu),
    .ALUResult(ALU_result),
    .zero(zero),
    .equalComp(equal_comp)
);

mux_N_bit #(32) jumper (
    .in0(register_write_data),
    .in1(pc_plus4),
    .mux_out(write_data),
    .control( jump)
);

mux_N_bit #(32) ALU_mux (
    .in0(read_data_2),
    .in1(immediates),
    .mux_out(ScrB),
    .control( ALUSrc)
);

mux_N_bit #(32) data_memory_mux (
    .in0(ALU_result),
    .in1(read_data),
    .mux_out(register_write_data),
    .control(mem_reg)
);

mux_N_bit #(32) branching_mux (
    .in0(pc_plus4),
    .in1(branch_out),
    .mux_out(pc_in),
    .control(branch_zero)
);

and_gate branching_and(
    .branch(branch),
    .zero(zero),
    .branch_zero(branch_zero)
);

alu_add_only program_counter_4 (
    .in_a(pc_out),
    .in_b($signed(32'b0100)),
    //in_b(32'h0004),
    .add_out(pc_plus4)
); // pc + 4

```

```

alu_add_only pc_branching (
    .in_a(pc_out),
    .in_b(immediate),
    .add_out(branch_out)
);

endmodule

// -----CONTROLLER-----

module maincontroller( control_signal, Opcode, Aluop, RegWrite, MemWrite, MemRead, Branch,
ALUSrc, Alu0, Alu1, jump, ALU_En, mem_reg);
    input [6:0] Opcode;
    output [1:0] Aluop; //ALUSrc, MemtoReg, RegWrite, MemRead, MemWrite, Branch, jump,
    output reg [9:0] control_signal;
    output wire RegWrite, MemWrite, MemRead, Branch, ALUSrc, Alu0, Alu1, jump, ALU_En,
mem_reg;
    assign {RegWrite, MemWrite, MemRead, Branch, ALUSrc, Alu0, Alu1, jump, ALU_En,
mem_reg} = control_signal;
    assign Aluop = {Alu0, Alu1};
    always @(*)
    begin
        case(Opcode)
            7'b0110011 : control_signal <= 10'b1000000000; // R-type
            7'b0000011 : control_signal <= 10'b1010110000; // I-type load
            7'b0010011 : control_signal <= 10'b1000101000; // I-type imm
            7'b0100011 : control_signal <= 10'b0100110001; // s-type
            7'b1100011 : control_signal <= 10'b0001011000; // sb-type
            7'b1101111 : control_signal <= 10'b10001xx110; // jal-type
            7'b0110111 : control_signal <= 10'b10001xx010; // lui-type
            7'b0010111 : control_signal <= 10'b00000xx010; // auipc-type
            default : control_signal <= 10'b0000000010;
        endcase
    end

endmodule

```

```
// -----INSTRUCTION_PARSER-----
```

```
module instruction_parser(
```

```
    input [31:0] instruction,  
    output reg [4:0] rs1,  
    output reg [4:0] rs2,  
    output reg [4:0] rd,  
    output reg [6:0] opcode,  
    output reg [31:0] imm,  
    output reg [3:0] func
```

```
);
```

```
always @(*)
```

```
begin
```

```
    opcode = instruction[6:0]; // extract opcode
```

```
    case(opcode)
```

```
        7'b0110011 : // R-type
```

```
        begin
```

```
            rd = instruction[11:7];
```

```
            rs1 = instruction[19:15];
```

```
            rs2 = instruction[24:20];
```

```
            imm = 32'hx;
```

```
            func = {instruction[14:12],instruction[30]};
```

```
        end
```

```
        7'b0000011 : // I-type load
```

```
        begin
```

```
            rd = instruction[11:7];
```

```
            rs1 = instruction[19:15];
```

```
            rs2 = instruction[24:20];
```

```
            imm = $signed(instruction[31:20]);
```

```
            func = {instruction[14:12],instruction[30]};
```

```
        end
```

```
        7'b0010011 : // I-type imm
```

```
        begin
```

```
            rd = instruction[11:7];
```

```
            rs1 = instruction[19:15];
```

```
            rs2 = 5'hx;
```

```
            imm = $signed(instruction[31:20]);
```

```
            func = {instruction[14:12],instruction[30]};
```

```

end

7'b0100011 : // s-type
begin
    rd = instruction[11:7];
    rs1 = instruction[19:15];
    rs2 = instruction[24:20];
    imm = $signed({instruction[31:25],instruction[11:7]});
    func = {instruction[14:12],instruction[30]};
end

7'b1100011 : // sb-type
begin
    rd = 5'hx;
    rs1 = instruction[19:15];
    rs2 = instruction[24:20];
    imm = $signed({instruction[31],instruction[7],instruction[30:25],instruction[11:8],1'b0});
    func = {instruction[14:12],instruction[30]};
end

end

7'b1101111 : // jal-type
begin
    rd = instruction[11:7];
    rs1 = 5'hx;
    rs2 = 5'hx;
    imm =
$signed({instruction[20],instruction[10:1],instruction[11],instruction[19:12]});
    func = 4'hx;
end

end

7'b0110111 : // lui-type
begin
    rd = instruction[11:7];
    rs1 = 5'hx;
    rs2 = 5'hx;
    imm = $signed(instruction[31:12]);
    func = 4'hx;
end

```

```

        end

        7'b0010111 : // auipc-type
        begin
            rd = instruction[11:7];
            rs1 = 5'hx;
            rs2 = 5'hx;
            imm = $signed(instruction[31:12]);
            func = 4'hx;
        end

    endcase

end
endmodule

// -----ALU-----

`timescale 1ns/100ps

module alu (ScrA,ScrB,alu_control,ALUResult,zero,equalComp);
    input [31:0] ScrA,ScrB;
    input [3:0] alu_control;
    output reg [31:0] ALUResult;
    output reg zero;
    input [1:0]equalComp;

    wire equal_inequal;
    wire Comparatorenable;

    assign {equal_inequal,Comparatorenable} = equalComp;

always @ (*)
begin

    ALUResult='d0;
    zero='b0;

    case(alu_control)
    4'b0000: begin//AND

```



```

        zero=0;
        ALUResult = ScrA & ScrB;
    end
    4'b0001: begin//OR
        zero=0;
        ALUResult = ScrA | ScrB;
    end
    4'b0010: begin//ADD
        zero=0;
        ALUResult = ScrA + ScrB;
    end
    4'b0011: begin//XOR
        ALUResult = ScrA ^ ScrB;
        zero=0;
        if (Comparatorenable=='b1') begin
            if (equal_inequal=='b1') begin
                zero=(ALUResult==32'b0);
            end
            else begin
                zero=(ALUResult!=32'b0);
            end
        end
    end
    4'b0100:begin//SLL
        ALUResult = ScrA << ScrB;
    end
    4'b0101:begin//SLT set less than
        ALUResult = ($signed(ScrA) < $signed(ScrB));// less than Correction
        if (Comparatorenable=='b1') begin
            if (equal_inequal=='b1') begin
                zero=(ALUResult!=32'b0);
            end else begin
                zero=(ALUResult==32'b0);
            end
        end
    end
    4'b0110://SUB
        begin
        ALUResult = $signed (ScrA)-$signed(ScrB);
        zero = ($signed(ALUResult)==$signed(1'd0));
        end
    4'b0111://SLTU
        begin
        ALUResult=(ScrA<ScrB);

```

```

        if (Comparatorenable=='b1') begin
            if (equal_inequal=='b1') begin
                zero=(ALUResult!=32'b0);
            end else begin
                zero=(ALUResult==32'b0);
            end
        end
    end
end
4'b1000:begin//SRL
    ALUResult = ScrA >> ScrB;
end
4'b1001:begin//SRLA
    ALUResult = $signed(ScrA) >>> ScrB;
end

default:begin
    ALUResult= 'b0;
end
endcase

end

endmodule

// -----ALU_CONTROLLER-----

module alu_control (alu_op, out_to_alu, funct, equal_comp, mem, ALU_En);
    input [1:0] alu_op;
    input ALU_En;
    input [3:0] funct;
    output [3:0] out_to_alu;
    output reg [1:0] equal_comp;
    output reg [2:0] mem;

    reg [3:0] out_to_alu;

    assign funct3 = {funct[3:1]};

    always @ (*)
    begin
        if (ALU_En == 'b0)begin
            equal_comp= 2'b00;

```

```

mem= 3'b000;
case (alu_op)
2'b00: //Rtype
    begin
        case(func)
        4'b0000:
            begin
                out_to_alu <= 4'b0010;
            end
        4'b0001:
            begin
                out_to_alu <= 4'b0110;
            end
        4'b1000:
            begin
                out_to_alu <= 4'b0011;
            end
        4'b1100:
            begin
                out_to_alu <= 4'b0001;
            end
        4'b1110:
            begin
                out_to_alu <= 4'b0000;
            end
        4'b0010:
            begin
                out_to_alu <= 4'b0100;
            end
        4'b1010:
            begin
                out_to_alu <= 4'b1000;
            end
        4'b1011:
            begin
                out_to_alu <= 4'b1001;
            end
        4'b0100:
            begin
                out_to_alu <= 4'b0101;
            end
        4'b0110:
            begin
                out_to_alu <= 4'b0111;
            end
        end
    end
end

```

```

                                end
                                endcase
                                end
2'b01:
    begin
        case(func3)
            3'b000:
                begin
                    out_to_alu <= 4'b0010;
                end
            3'b100:
                begin
                    out_to_alu <= 4'b0011;
                end
            3'b110:
                begin
                    out_to_alu <= 4'b0001;
                end
            3'b111:
                begin
                    out_to_alu <= 4'b0000;
                end
            3'b001:
                begin
                    out_to_alu = 4'b0100;
                end
            3'b101:
                begin
                    if (func3[0]==0)
                        out_to_alu <= 4'b1000;
                    else
                        out_to_alu <= 4'b1001;
                    end
                end
            endcase
        end
2'b10:
    begin
        case(func3)
            3'b000:
                begin
                    out_to_alu <= 4'b0010;

```

```

        mem<= 3'b001;
    end
    3'b001:
    begin
        out_to_alu <= 4'b0010;
        mem<= 3'b010;
    end
    3'b010:
    begin
        out_to_alu <= 4'b0010;
        mem<= 3'b011;
    end
    3'b100:
    begin
        out_to_alu <= 4'b0010;
        mem<= 3'b101;
    end
    3'b101:
    begin
        out_to_alu <= 4'b0010;
        mem<= 3'b011;
    end
    endcase
end
2'b11:
begin
    case(func3)
    3'b000:
    begin
        out_to_alu <= 4'b0011;
        equal_comp <= 2'b11;
    end
    3'b001:
    begin
        out_to_alu <= 4'b0011;
        equal_comp <= 2'b10;
    end
    3'b100:
    begin
        out_to_alu <= 4'b0101;
        equal_comp <= 2'b11;
    end
    3'b101:

```

```

        begin
            out_to_alu <= 4'b0101;
            equal_comp <= 2'b10;
        end
        3'b110:
        begin
            out_to_alu <= 4'b0111;
            equal_comp <= 2'b11;
        end
        3'b111:
        begin
            out_to_alu <= 4'b0111;
            equal_comp <= 2'b10;
        end
    endcase
end

    endcase
end
endmodule

// -----ALU_ADD_ONLY-----

module alu_add_only (in_a, in_b, add_out);
    input [31:0] in_a, in_b;
    output [31:0] add_out;
    assign add_out=in_a+in_b;
endmodule

// -----AND_GATE-----

module and_gate (input branch, zero, output branch_zero);
    assign branch_zero = branch & zero;
endmodule

// -----INSTRUCTION_MEMORY-----

module data_memory (addr, write_data, read_data, clk, mem_read, mem_write, DATA_MEM_In);

    input [31:0] addr;
    input [31:0] write_data;
    input clk, mem_read, mem_write;

```

```

input [2:0] DATA_MEM_In;
output reg [31:0] read_data;

reg [31:0] dmemory [63:0];
reg [31:0] write_data_in;

wire [5:0] shifted_addr;
wire [2:0] DATA_MEM_In;
wire [31:0] DATA;

assign shifted_addr = addr[5:0];

//assign DATA = dmemory[addr];

always @(posedge clk)
begin
    if (mem_read == 1'b1)

        begin

            case(DATA_MEM_In)
            3'b001: begin
                read_data = $signed(dmemory[shifted_addr][7:0]);

                end

            3'b010:begin
                read_data = $signed(dmemory[shifted_addr][15:0]);
                end

            3'b011: read_data = dmemory[shifted_addr];
            3'b101: read_data = $unsigned(dmemory[shifted_addr][7:0]);
            3'b110: read_data= $unsigned(dmemory[shifted_addr][15:0]);
            endcase

        end

    else if (mem_write == 1'b1)

        begin

            case(DATA_MEM_In)
            3'b001: begin
                write_data_in = $signed(write_data[7:0]);

```

```

        dmemory[shifted_addr] = write_data_in;
    end
    3'b010:begin
        write_data_in = $signed(write_data[15:0]);
        dmemory[shifted_addr] = write_data_in;
    end

    3'b011:begin
        dmemory[shifted_addr] = write_data;
    end
endcase
end

end

endmodule

// -----INSTRUCTION_MEMORY-----

module instruction_memory (read_addr, instruction, clk);
    input clk;
    input [31:0] read_addr;
    output [31:0] instruction;
    reg [31:0] Imemory [63:0];
    integer k;

    wire [7:0] shifted_read_addr;
    assign shifted_read_addr = read_addr[7:0] >>> 2;
    assign instruction = Imemory[shifted_read_addr];

    always @(posedge clk)
    begin

        for (k=16; k<32; k=k+1) begin// here Ou changes k=0 to k=16
            Imemory[k] = 32'b0;
        end
        Imemory[0] = 32'b00000000111100000000000010010011;
        Imemory[1] = 32'b00000000111100000000000010010011; //addi x1, x0, 15 - I
        Imemory[2] = 32'b000000001010000000000000100010011; //addi x2, x0, 10 - I
        Imemory[3] = 32'b000000000001000100000000110110011; //add x3, x2, x1 - R
        Imemory[4] = 32'b00000000000100010111001000110011; //and x4, x2, x1 - R
        Imemory[5] = 32'b0000000000010001011001010110011; //or x5, x2, x1 - R
    end
end

```



```

Imemory[6] = 32'b00000000010000011010000000100011; //sw x4, 0(x3)
Imemory[7] = 32'b00000000000000000000000000000000; //nop
Imemory[8] = 32'b00000000001100000010001000000011; //load x0, x4, 3
Imemory[9] = 32'b00000000000000000000000000000000; //nop

Imemory[10] = 32'b000000000101000000000001100010011; //addi x6, x0, 10 - I
Imemory[11] = 32'b00000000001000110000010001100011; //bne x6, x2, 8
Imemory[12] = 32'b00000000111100000000000010010011; //addi x1, x0, 15 <Skipped
Imemory[13] = 32'b00000000000000000000000000000000; //nop

```

```

end

```

```

endmodule

```

```

// -----N_BIT_MUX-----

```

```

module mux_N_bit (in0, in1, mux_out, control);
    parameter N = 32;
    input [N-1:0] in0, in1;
    output [N-1:0] mux_out;
    input control;
    assign mux_out=control?in1:in0;
endmodule

```

```

// -----PROGRAM_COUNTER-----

```

```

module program_counter (clk, reset, pc_in, pc_out);
    input clk, reset;
    input [31:0] pc_in;
    output [31:0] pc_out;
    reg [31:0] pc_out;
    always @ (posedge clk or posedge reset)
    begin
        if(reset==1'b1)
            pc_out<=0;
        else
            pc_out<=pc_in;
        end
    end
endmodule

```

```

// -----TEST_BENCH-----

```

```

`timescale 1ns/100ps

```

```
module Itype_tb;

reg clk,reset;

Itype UUT (clk, reset, ALU_result);

initial
begin
    clk = 0;
    reset = 1;
    #15;reset = 0;
    #400
    $stop;
    //$finish;
end
always begin #10 clk=~clk; end
endmodule
```